
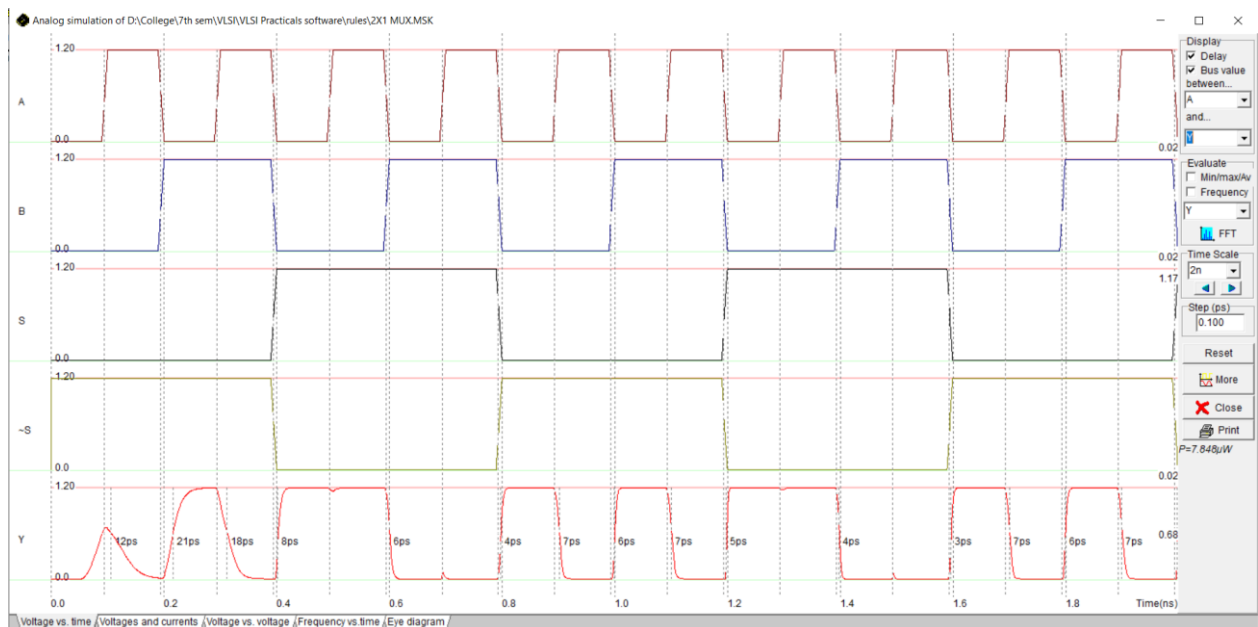


Outputs:

2:1 MUX USING LOGIC GATE

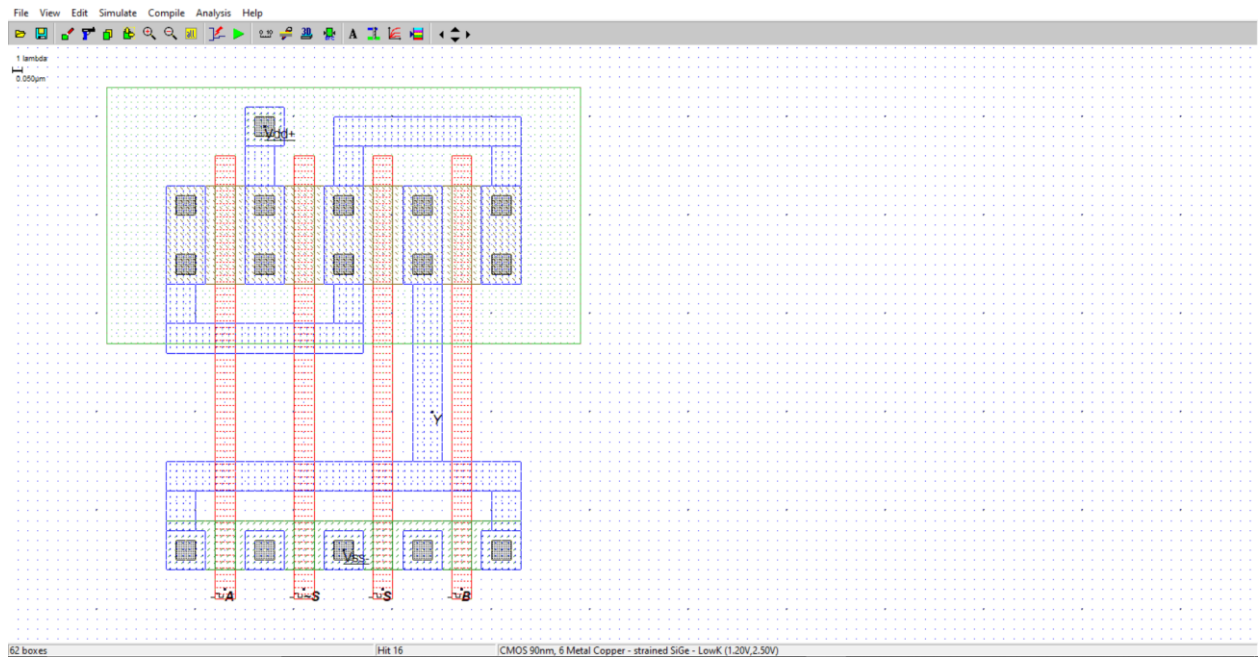

Output

2:1 MUX USING TRANSMISSION GATE

